

Bangladesh Army University of Science and Technology

Department of Computer Science and Engineering

Referred/Improvement/Backlog Examination, Fall 2018

Level-2 Term-II

Course Code: CSE 2205

Course Title: Digital Electronics and Pulse Technique

Time: 03 (Three) hours

Full Marks: 210


N.B. (i) Answer any three questions from each PART
(iii) Marks allotted are indicated in the margin

(ii) Use separate answer script for each PART
(iv) Symbols have their usual meanings

PART A

(Answer any three questions)

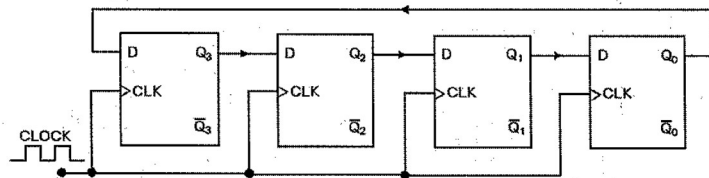1. a) What is Digital Electronics? Write down five advantages of Digital Electronics. 5+10
b) Define Diode. Draw 2-input diode AND and OR logic gates. 5+10
c) Write down three leads (legs) name of transistor explain why they are used for? 5
2. a) Write down classification of Digital logic families in a block diagram. 10
b) Briefly explain the operation of TTL NOR gate and CMOS OR gate. 5+5
c) Write down types of Flip-flop? Differentiate latches from flip-flops? 5+10
3. a) Define the terms: (i) Propagation delay, (ii) Fan-in, (iii) Fan-out and (iv) Noise margin 12
b) Describe the operation of the following circuits diagram: 8



- c) What is Counter? Design 3-Bit Synchronous Counter from excitation and truth table of J-K Flip Flop. 3+12
4. a) What is Universal Shift Register? What is it used for? 6
b) Describe 4-bit Bidirectional shift register operation with block diagram. 10
c) Write short notes on : (i) ROM, (ii) PAL and (iii) PLA 9
d) Draw the PAL circuit diagram for the following equations 10

$$F1 = C' + A'B'$$


$$F2 = A'BC' + AC + AB'$$

$$F3 = AD + BD + F1$$


$$F4 = AB + CD + F1'$$

PART B
(Answer any three questions)

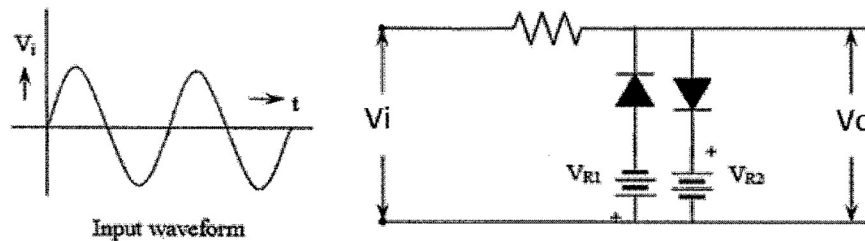5. a) State the purpose of ADC and DAC. 10
 b) Why is PCM used? Describe Sampling, Holding, Quantization, and Binary Encoding steps of PCM with appropriate diagram. 20
 c) Explain the operation of a binary weighted resistor of DAC. 5
6. a) Define and describe Clipper and Clamper with Circuit diagrams. 10
 b) What if filter? Describe operation of RC low pass filter where $RC \gg T$ and RC high pass filter where $RC \ll T$ with circuit diagrams and expected output wave shapes. 5+10
 c) Draw the output wave to the circuit shown in the figure below: 10



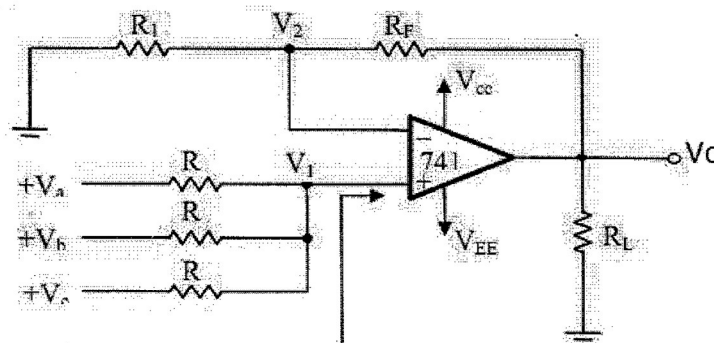7. a) What do you mean by Multivibrator? Describe monostable Multivibrator with circuit diagram. 5+10
 b) Define oscillator. Write its application areas. 5+5
 c) What are the features of a Schmitt trigger? Represent a scenario where Schmitt trigger performs better than a normal comparator. 10
8. a) What is Op-amp? Describe the operation of the following circuit diagram. 5+5



- b) What is V_{out} for summing amplifier and averaging amplifier if the input voltage are +5.0V, -3.0V and +4.5V and all resistors are $10k\Omega$. 10
 c) Determine R_1 , R_2 and V_{ref} , if $UPT=2.5V$, $LTP=1.0V$ and $V_{sat}=12V$. 9
- d) Write down uses and advantages of pulse transformer. 6