

# Bangladesh Army University of Science and Technology

## Department of Computer Science and Engineering

Final Examination, Fall 2018

Course Code: CSE 2205

Time: 03 (Three) hours

Level-2 Term-II

Course Title: Digital Electronics and Pulse Technique

Full Marks: 210


N.B. (i) Answer any three questions from each PART  
(iii) Marks allotted are indicated in the margin

(ii) Use separate answer script for each PART  
(iv) Symbols have their usual meanings

### PART A

(Answer any three questions)

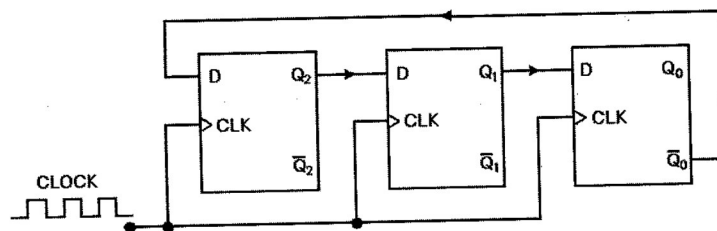1. a) What is Digital Electronics? Write down five advantages of Digital Electronics. 5+10  
b) Define Transistor. How NPN Transistor can work as a Switches. Describe its Operation 5+10  
c) Draw the basic circuit of a 2-input diode AND gate, and explain why. 5
2. a) Write down classification of Digital logic families in a block diagram. 10  
b) Briefly explain the operation of TTL NOR gate and CMOS OR gate. 5+5  
c) What is Flip-flops? Differentiate latches from flip-flops? Why latches are introduced? 5+10
3. a) Define the terms: (i) propagation delay, (ii) fan-in, (iii) fan-out and (iv) Noise margin 12  
b) Describe the operation of the following circuits diagram: 8




- c) What is a Counter? Design a 3-Bit Synchronous Counter from excitation and truth table of J-K flip-flop. 3+12
4. a) What is Universal Shift Register? Why is it used? 5  
b) Describe 4-bit universal shift register operation with block diagram. 10  
c) Write short notes on : (i) ROM, (ii) PAL and (iii) PLA 15  
d) Draw the PLA circuit diagram for the following equations 5  
$$F1 = AB + BC + AC$$
$$F2 = (AB + A'B')'$$

### PART B

(Answer any three questions)


5. a) State the purpose of ADC and DAC. 10  
b) Why PCM is used? Describe the steps of PCM with appropriate diagram. 20  
c) Explain the operation of a 4-bit R-2R ladder DAC. 5

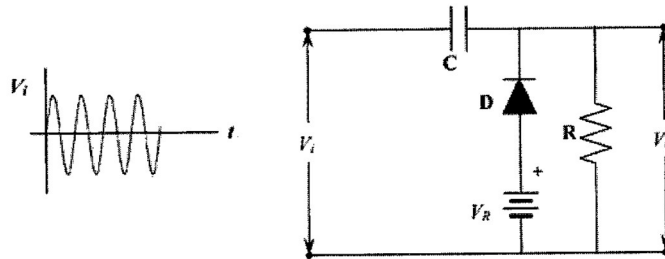6. a) Define and describe Clipper and Clamper with Circuit diagrams. 10  
 b) What if filter? Describe operation of RC low pass filter where  $RC \gg T$  and RC high pass filter where  $RC \ll T$  with circuit diagrams and expected output wave shapes. 5+10  
 c) Draw the output wave to the circuit shown in the figure below: 10



7. a) What do you mean by Multivibrator? Describe astable Multivibrator with circuit diagram. 5+10  
 b) Define oscillator. Write its classification and application areas. 5+5  
 c) What are the features of a Schmitt trigger? Represent a scenario where Schmitt trigger performs better than a normal comparator. 10

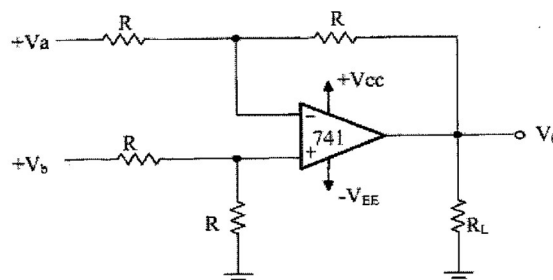8. a) What is Op-amp? Describe the operation of the following circuit diagram. 5+5



- b) What is  $V_{out}$  for summing amplifier and averaging amplifier if the input voltage are +5.0V, -3.0V and +4.5V and all resistors are  $10k\Omega$ . 10  
 c) Calculate the input voltage  $V_{in}$ , if  $UTP=2.5$ ,  $LTP=1.0$  and  $V_{SAT}=12V$ . 9  
 d) Write down uses and advantages of pulse transformer. 6